



RF IMPEDANCE AND THE SMITH CHART

JEREMY HALEY, WG9T

LONGMONT AMATEUR RADIO CLUB

RESISTANCE, REACTANCE, AND IMPEDANCE

RESISTANCE Energy conversion to heat.


REACTANCE

Capacitance: Energy storage in electric field.

Inductance: Energy storage in magnetic field.

IMPEDANCE RESISTANCE + REACTANCE

POLAR PLOT OF REFLECTION COEFFICIENT

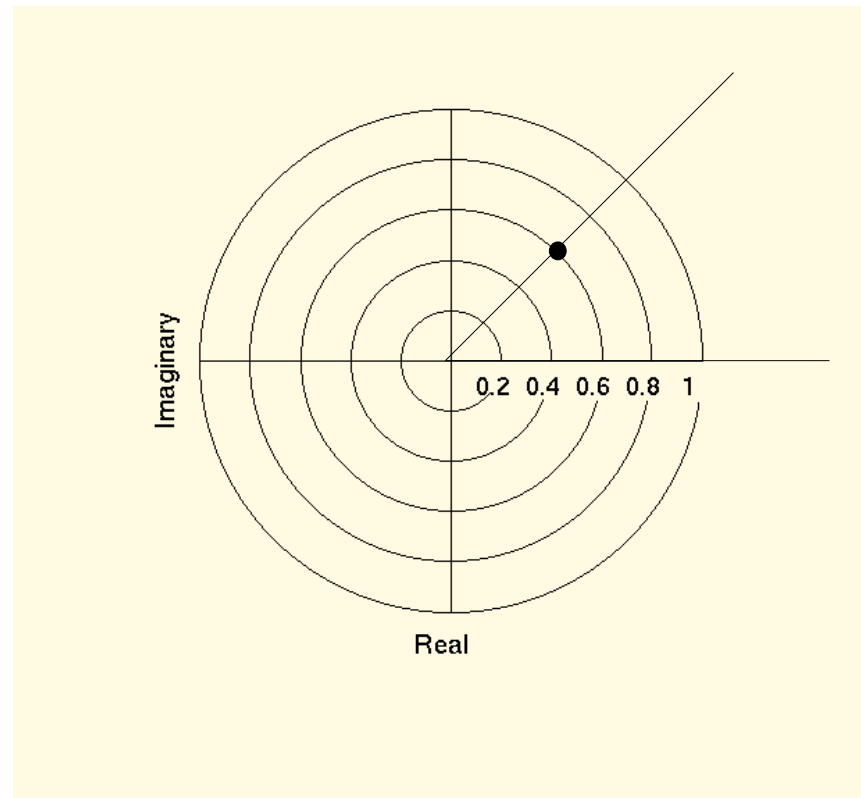


ReflCoeff.
= 0.6 magnitude,
angle 45 degrees.

Voltage Waves: forward and reflected relative to a fixed reference point (e.g. SWR meter in the shack).

Reflection Coefficient = (refl. voltage) / (fwd. voltage)
[n.a.]

Voltages have amplitude [V] and phase angle [degrees].

OVERLAY IMPEDANCE COORDINATES

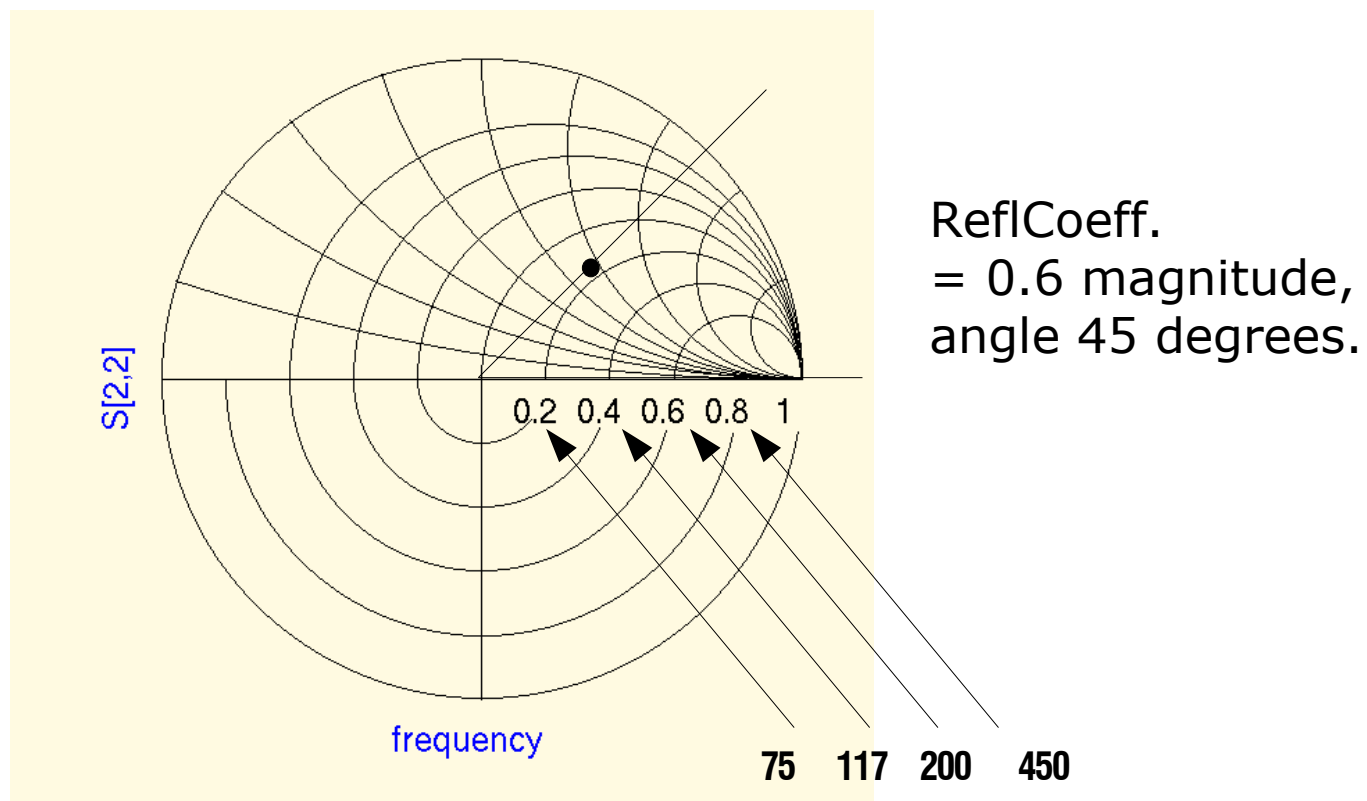

Equation relates impedance to reflection coefficient.


$$Z = Z_{\text{ref}} * ((1 + \text{ReflCoeff.}) / (1 - \text{ReflCoeff.})) \text{ [Ohm]}$$

Reference impedance, Z_{ref} is typically 50 ohms.

RESISTANCE & REACTANCE CIRCLES

Resistance constant along these circles.

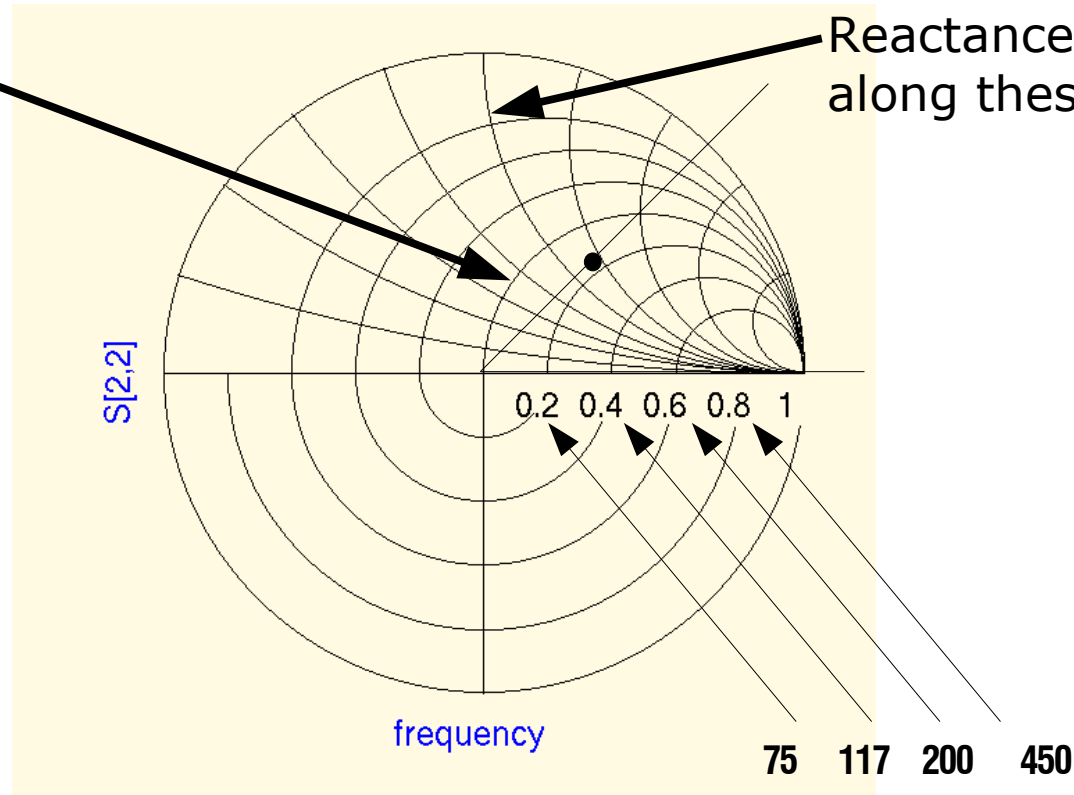Reactance constant along these circles (arcs).




Upper half of impedance map: inductive reactance and resistance.

Lower half of impedance map: capacitive reactance and resistance.

SMITH CHART FOR IMPEDANCE

NOTICE THAT
IMPEDANCE
IS
NORMALIZED.
50 >>> 1

FROM
EXAMPLE
IN ARRL
ANTENNA
BOOK

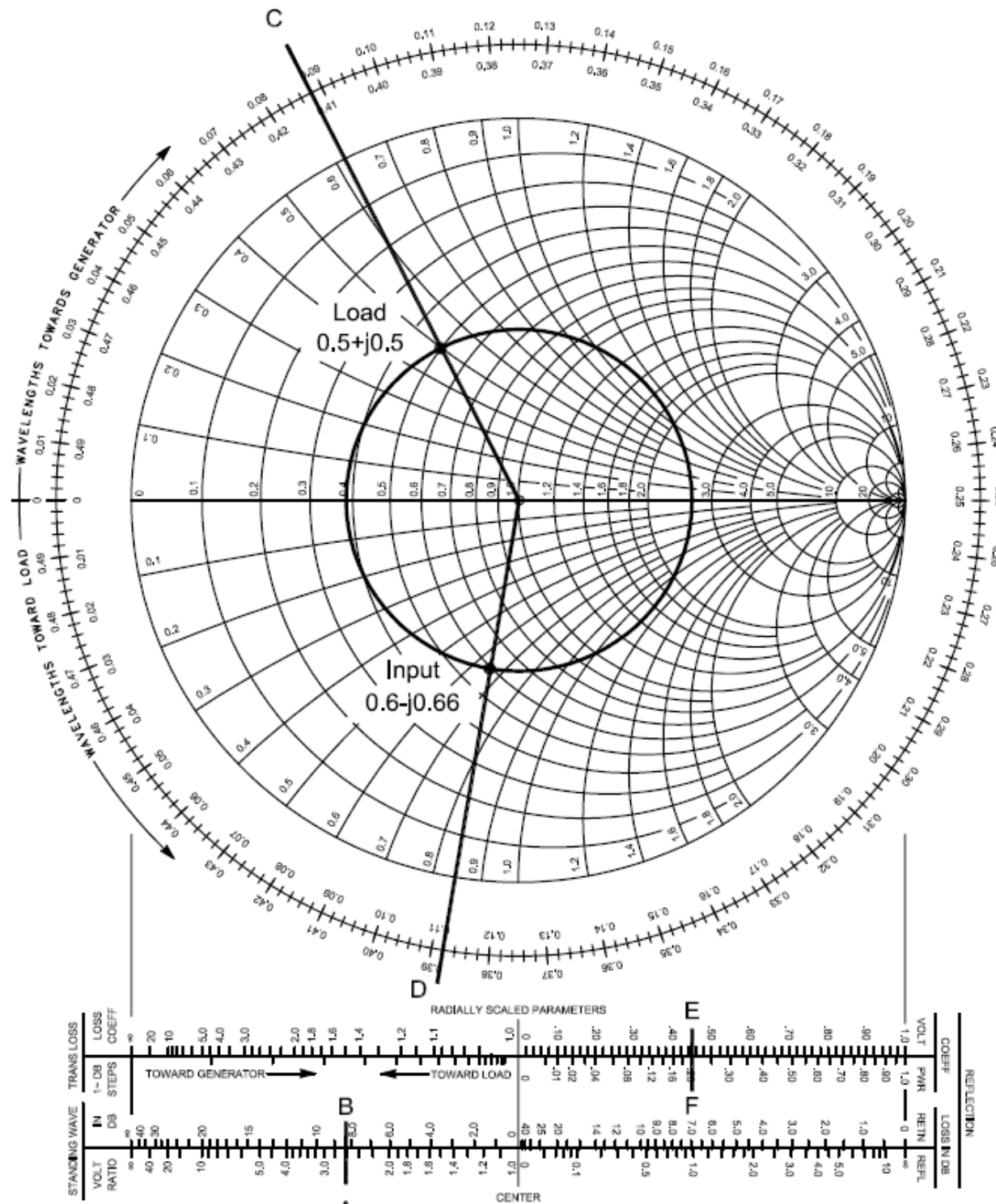

COMPUTER TOOL ALTERNATIVE TO COMPASS AND STRAIGHTEDGE

Free open-source cross-platform software: Quite Universal Circuit Simulator "QUCS"

- <http://qucs.sourceforge.net/>
- DC circuit analysis
- AC circuit analysis
- RF circuit analysis (S-parameter simulation)

EXAMPLE CIRCUIT "A"

Example from ARRL Antenna Book, Chapter 28.

Antenna impedance is given as $25 + j 25$ Ohm at some frequency.

The reactive portion $+j25$ Ohm indicates an inductive reactance.

Assume the frequency is 144.200 MHz.

What is the impedance at the radio end of a 0.3 wavelength long low-loss cable?

Assume the cable has a characteristic impedance (resistance) of 50 Ohms.

Simulate the circuit using the computer tool, and plot the result on the Smith Chart.

PC SIMULATION: CALCULATIONS AND DEFINITIONS

Equation

Eqn1

carrier_frequency_MHz=144.2

wavelength_air_meters=speed_of_light/(carrier_frequency_MHz*1E6)

speed_of_light=3E8

inductance_given_reactance=reactanceL_ohm/(2*pi*carrier_frequency_MHz*1E6)

line_physical_length_meters=0.3*wavelength_air_meters

reactanceL_ohm=25

swr_calc=rtoswr(S[3,3])

impedance_S11=rtoz(S[1,1])

impedance_S22=rtoz(S[2,2])

S parameter simulation

SP1

Type=const

Values=[144.2 MHz]

Parameter sweep

SW1

Sim=SP1




Type=lin

Param=phases


Start=0

Stop=180

Points=46

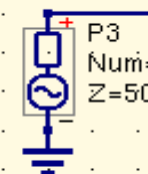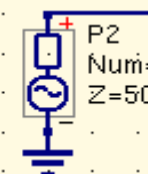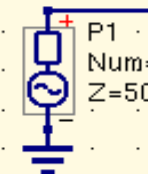

PC SIMULATION: SCHEMATIC

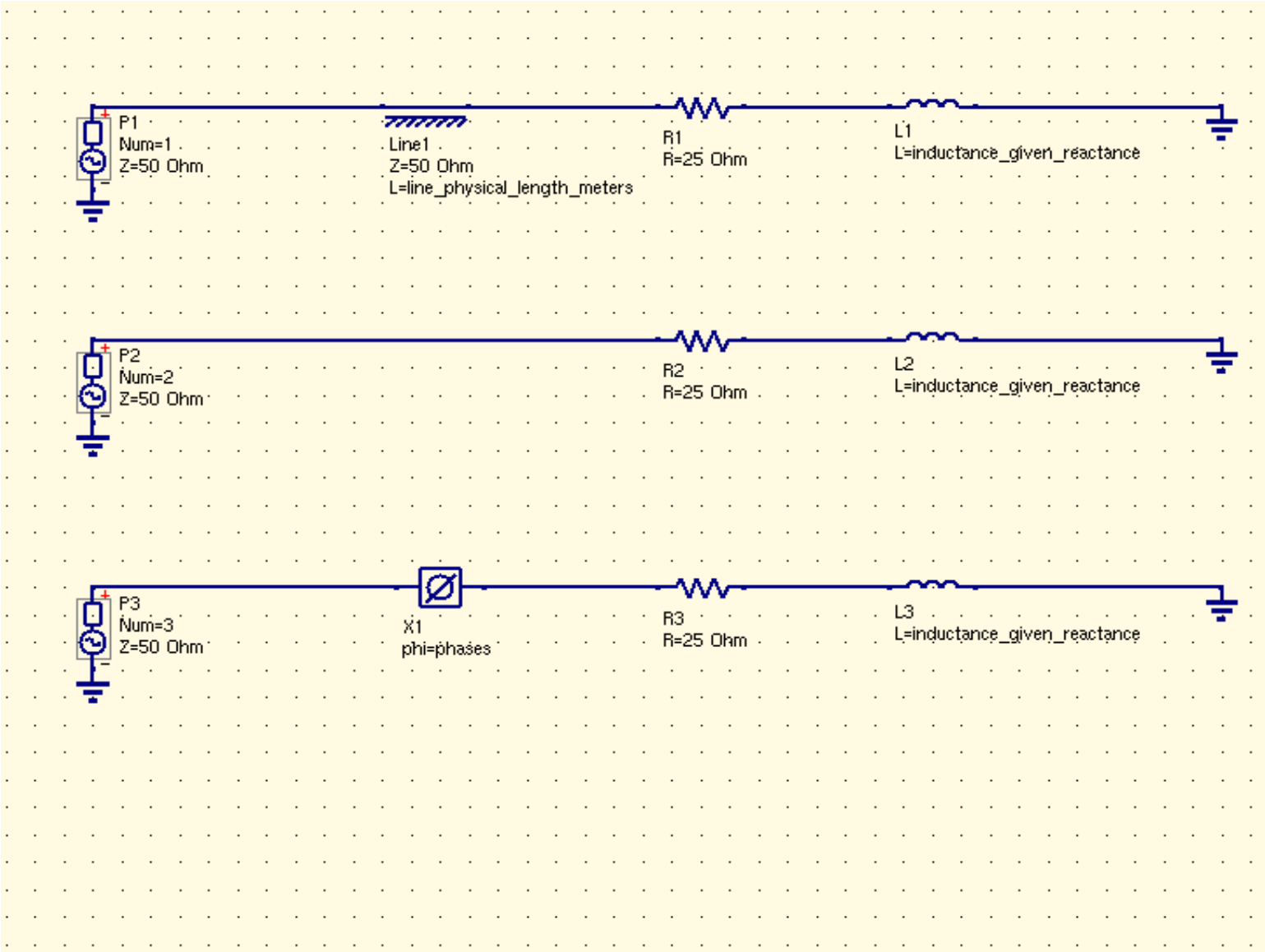

RESULTS: SMITH CHART PLOT


▲	phases	frequency	impedance_S22
■	0	1.44e8	25+j25
▼			

frequency: 1.44e+08
 phases: 0
 S[2,2]: -0.2+j0.4

frequency: 1.44e+08
 phases: 132
 S[2,3]: 0.419+j0.157

S[2,3]
 S[2,2]
 S[1,1]

▲	phases	frequency	swr_calc
■	0	1.44e8	2.62
▼			

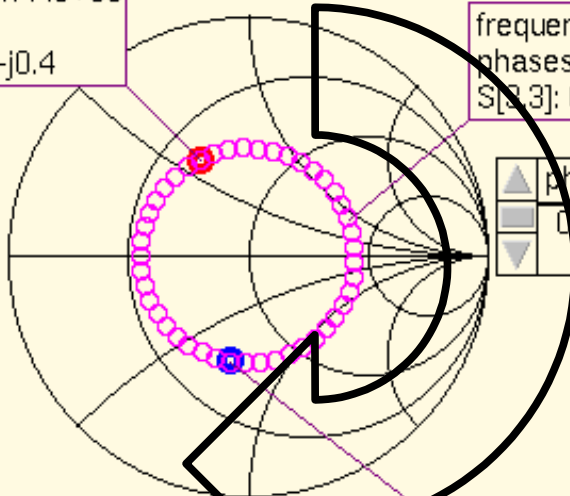

frequency
 frequency
 frequency

frequency: 1.44e+08
 phases: 0
 S[1,1]: -0.0745-j0.441

▲	phases	frequency	impedance_S11
■	0	1.44e8	29.7-j32.7
▼			

Rotation along 50 ohm line "Toward Generator (Radio)" 0.3 wavelengths.

EXAMPLE CIRCUIT "B"

Example from ARRL Antenna Book, Chapter 28.

Impedance measured at the radio end of a 2.35 wavelength long low-loss coaxial cable is $70 - j 25$ Ohm at some frequency.

The reactive portion $-j25$ Ohm indicates a capacitive reactance.

Assume the frequency is 144.200 MHz.

What is the impedance at the antenna feedpoint?

Assume the cable has a characteristic impedance (resistance) of 50 Ohms.

Simulate the circuit using the computer tool, and plot the result on the Smith Chart.

PC SIMULATION: CALCULATIONS AND DEFINITIONS

Equation

Eqn2

capacitance_given_reactance= $1/(2*\pi*carrier_frequency_MHz*1E6*reactanceC_ohm)$

line2_physical_length_meters= $-2.35*wavelength_air_meters$

reactanceC_ohm=25


swr_calc2= $rtoz(S[6,6])$

impedance_S44= $rtoz(S[4,4])$


impedance_S55= $rtoz(S[5,5])$

Using the computer simulation, negative cable lengths are possible. The negative value allows rotation along the SWR circle in the opposite direction.

PC SIMULATION: SCHEMATIC

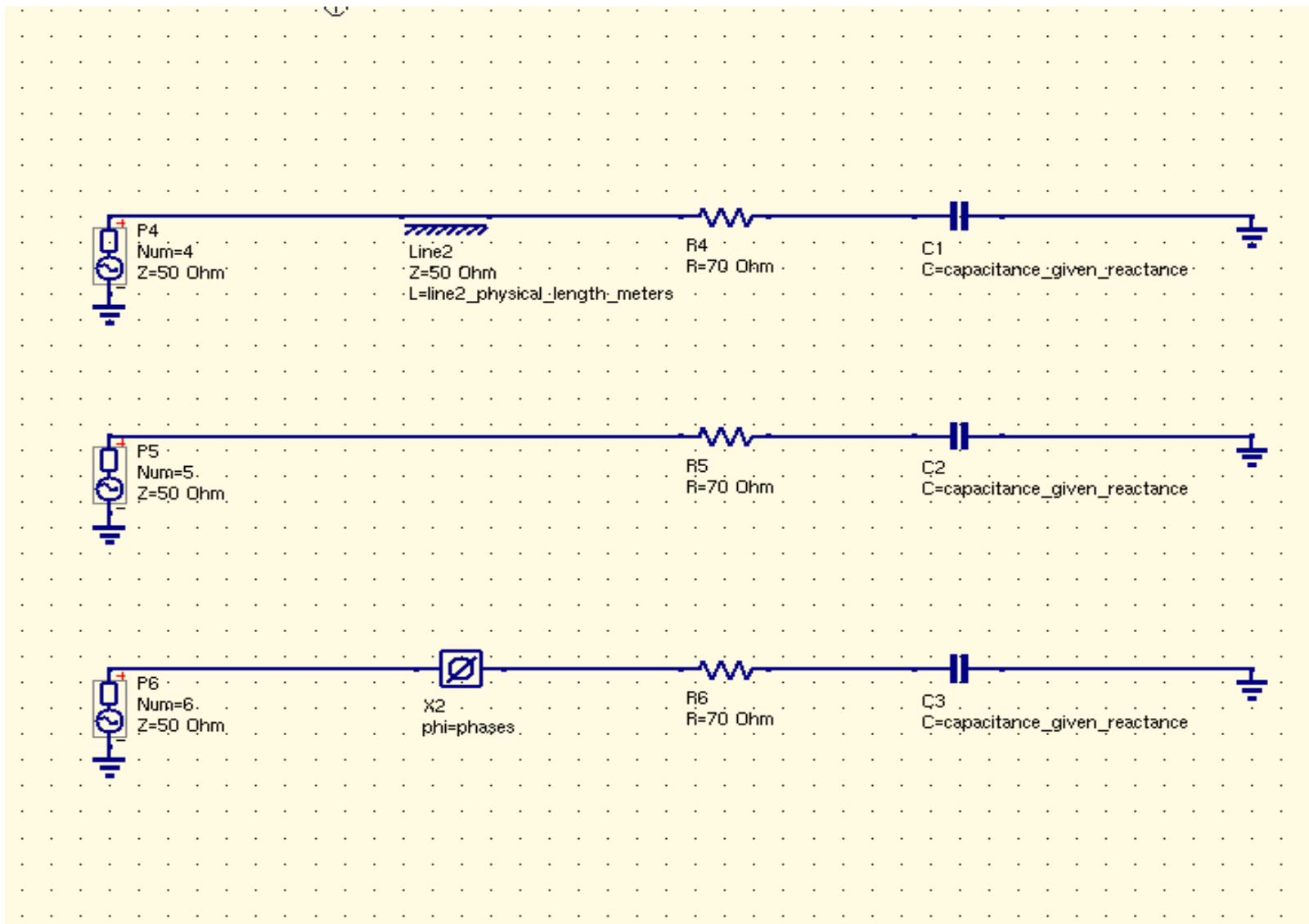

RESULTS: SMITH CHART PLOT

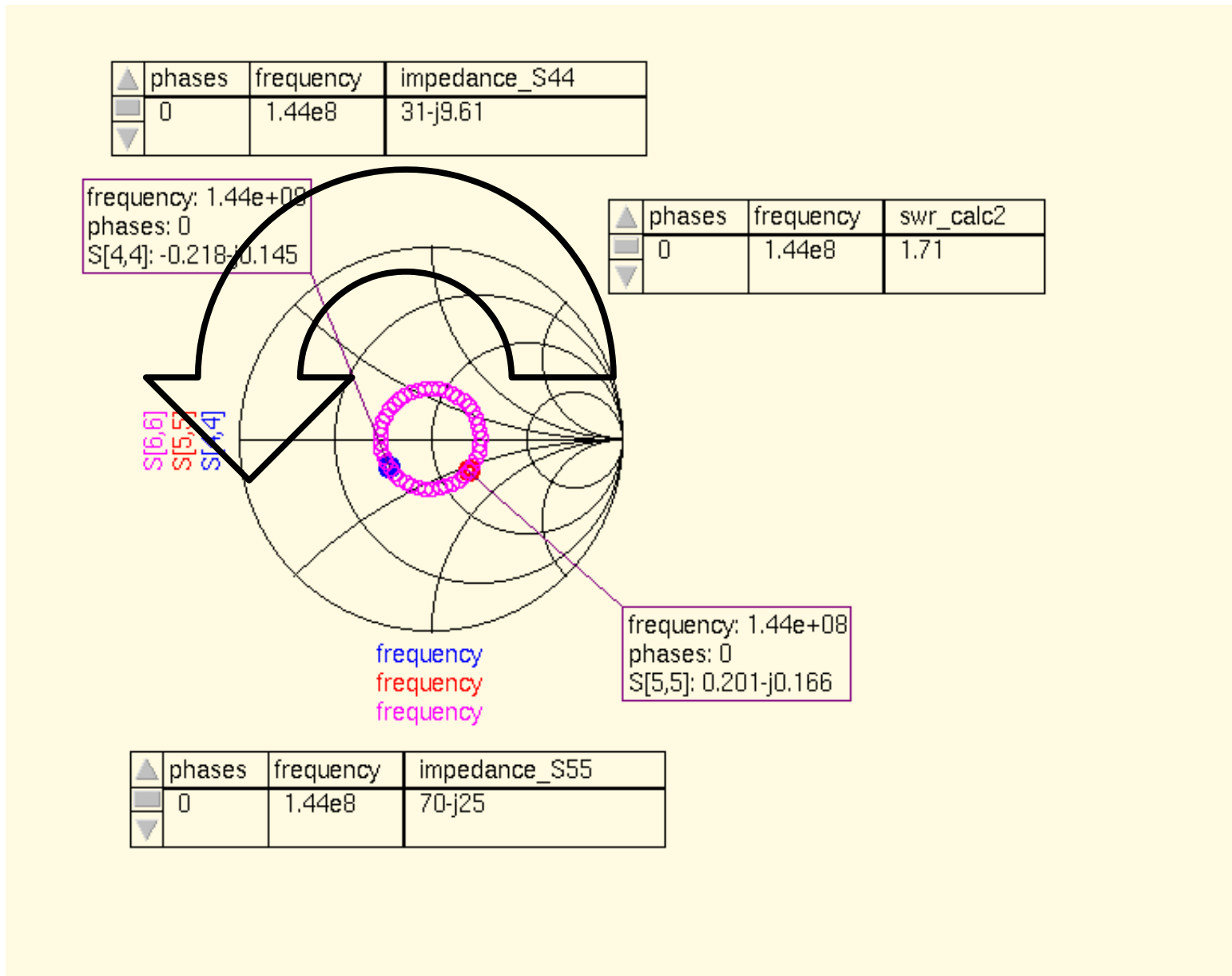

Rotation along 50 ohm line "Toward Load" 2.35 (4 times + 0.35)

EXAMPLE CIRCUIT "C"

An exact half-wavelength thin-wire dipole has been constructed from basic physics equations (instead of the more appropriate $468/f(\text{MHz})$ design equation).

Impedance data versus frequency for this antenna is plotted in a textbook for antenna engineers by Stutzman & Thiele.

Antenna is designed for 7.110 MHz.

For the following frequencies what is the impedance at the antenna feedpoint? 7.110 MHz, 14.110 MHz , and 18.110 MHz?

Simulate the circuit using the computer tool, and plot the result on the Smith Chart.

Try to design a simple inductance-capacitance matching circuit to improve the SWR, and plot the performance.

PC SIMULATION: SCHEMATIC 7.11 MHz, 73 + j 30 Ohms

Equation

Eqn1

carrier1_frequency_MHz=7.110

wavelength_air_meters=speed_of_light/(carrier1_frequency_MHz*1E6)

speed_of_light=3E8

inductance1_given_reactance=reactance1L_ohm/(2*pi*carrier1_frequency_MHz*1E6)

line_physical_length_meters=0.0*wavelength_air_meters

reactance1L_ohm=30

swr_calc=rtoswr(S[3,3])

impedance_S11=rtoz(S[1,1])

impedance_S22=rtoz(S[2,2])

**S parameter
simulation**

SP1

Type=const

Values=[7.11MHz]

**Parameter
sweep**

SW1

Sim=SP1

Type=lin


Param=phases

Start=0


Stop=180

Points=46

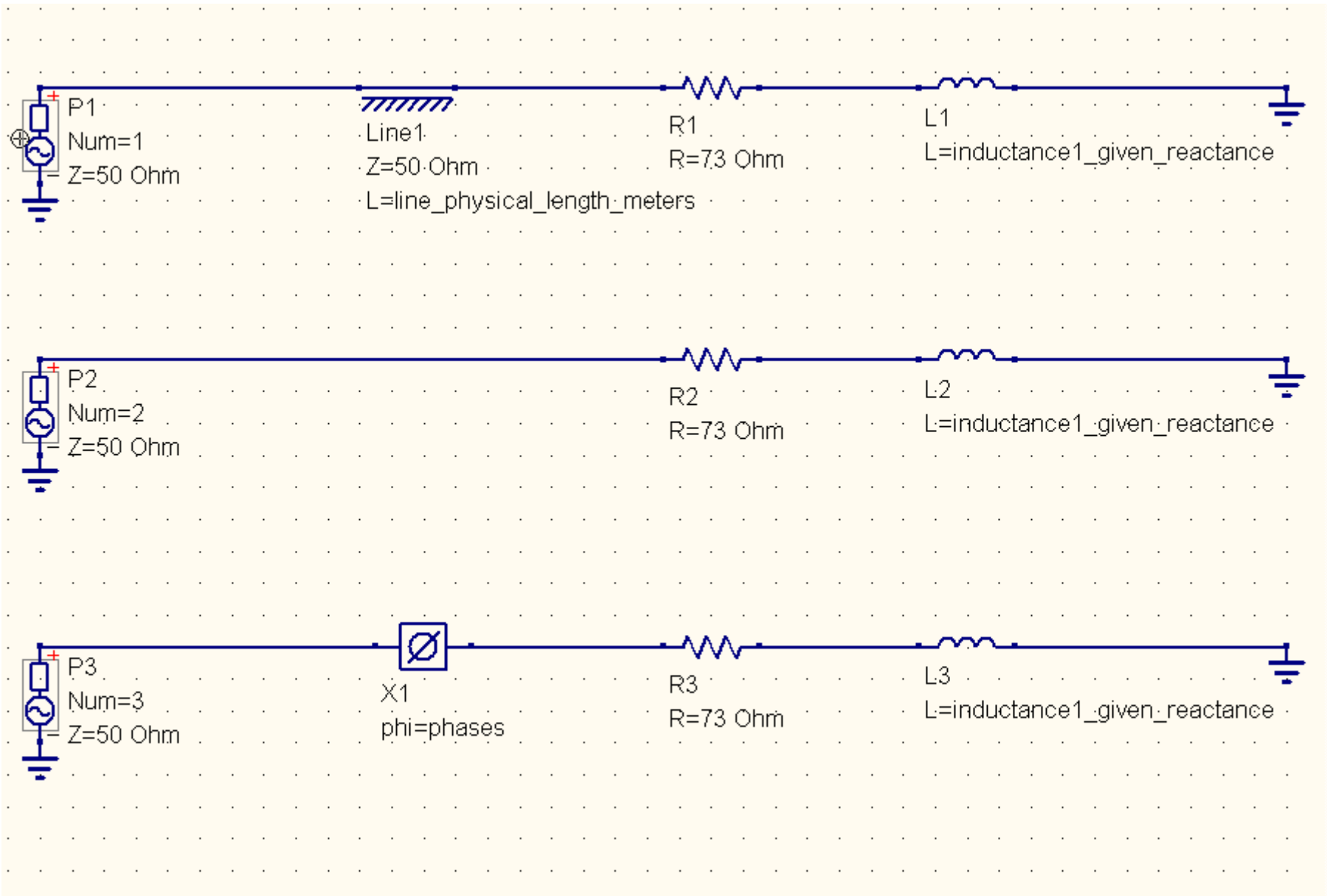PC SIMULATION: SCHEMATIC 7.11 MHz, 73 + j 30 Ohms



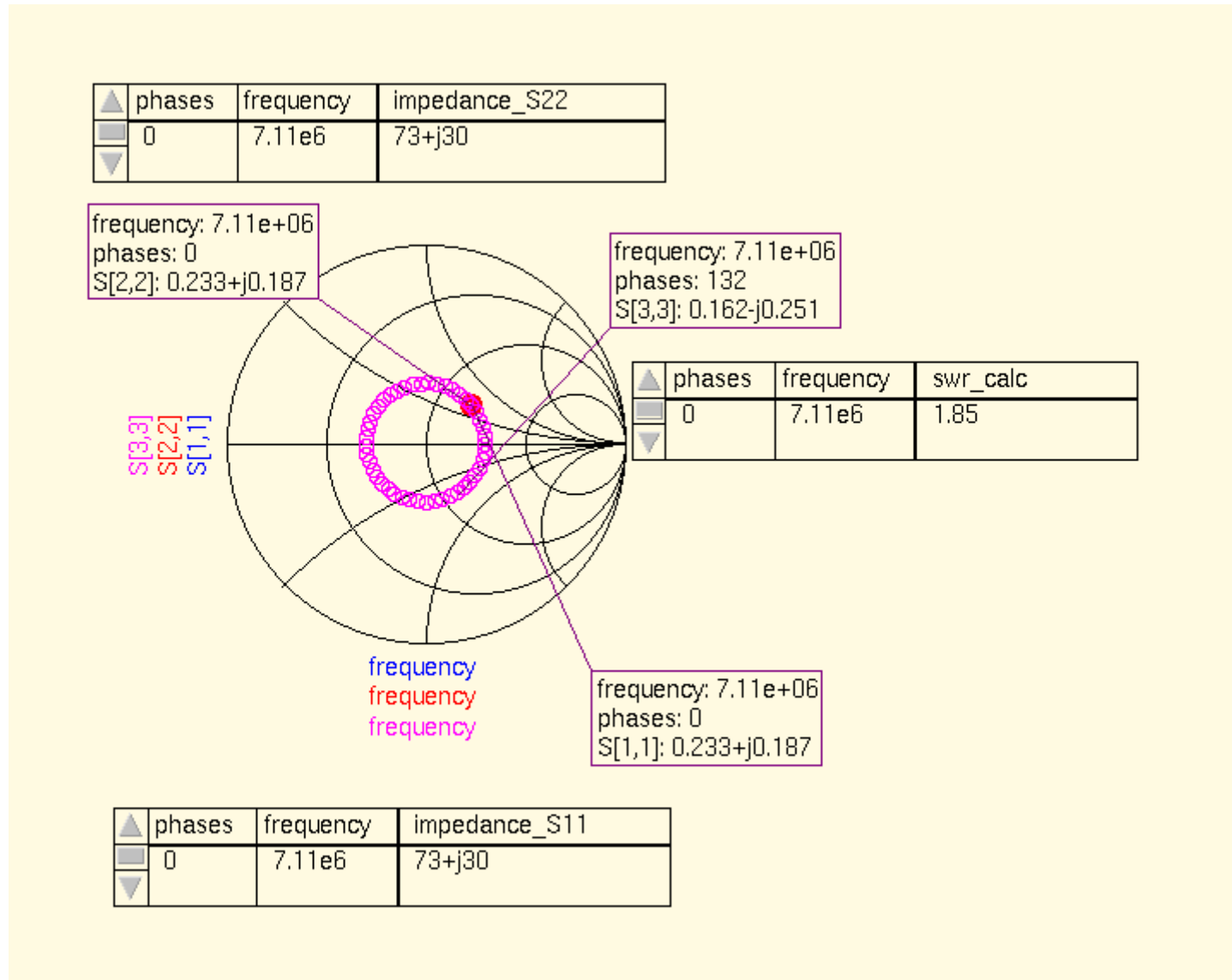RESULTS: SMITH CHART PLOT 7.11 MHz, 73 + j 30 Ohms



PC SIMULATION: SCHEMATIC 14.110 MHz, 1700 - j 1500 Ohm

S parameter simulation

SP1
Type=const
Values=[14.11 MHz]


Parameter sweep

SW1
Sim=SP1
Type=lin
Param=phases
Start=0
Stop=180
Points=46


Equation

Eqn2
capacitance_given_reactance= $1/(2*\pi*carrier2_frequency_MHz*1E6*reactanceC_ohm)$
carrier2_frequency_MHz=14.110
line2_physical_length_meters=0*wavelength_air_meters
reactanceC_ohm=1500
swr_calc2=rtoswr(S[6,6])
impedance_S44=rtoz(S[4,4])
impedance_S55=rtoz(S[5,5])

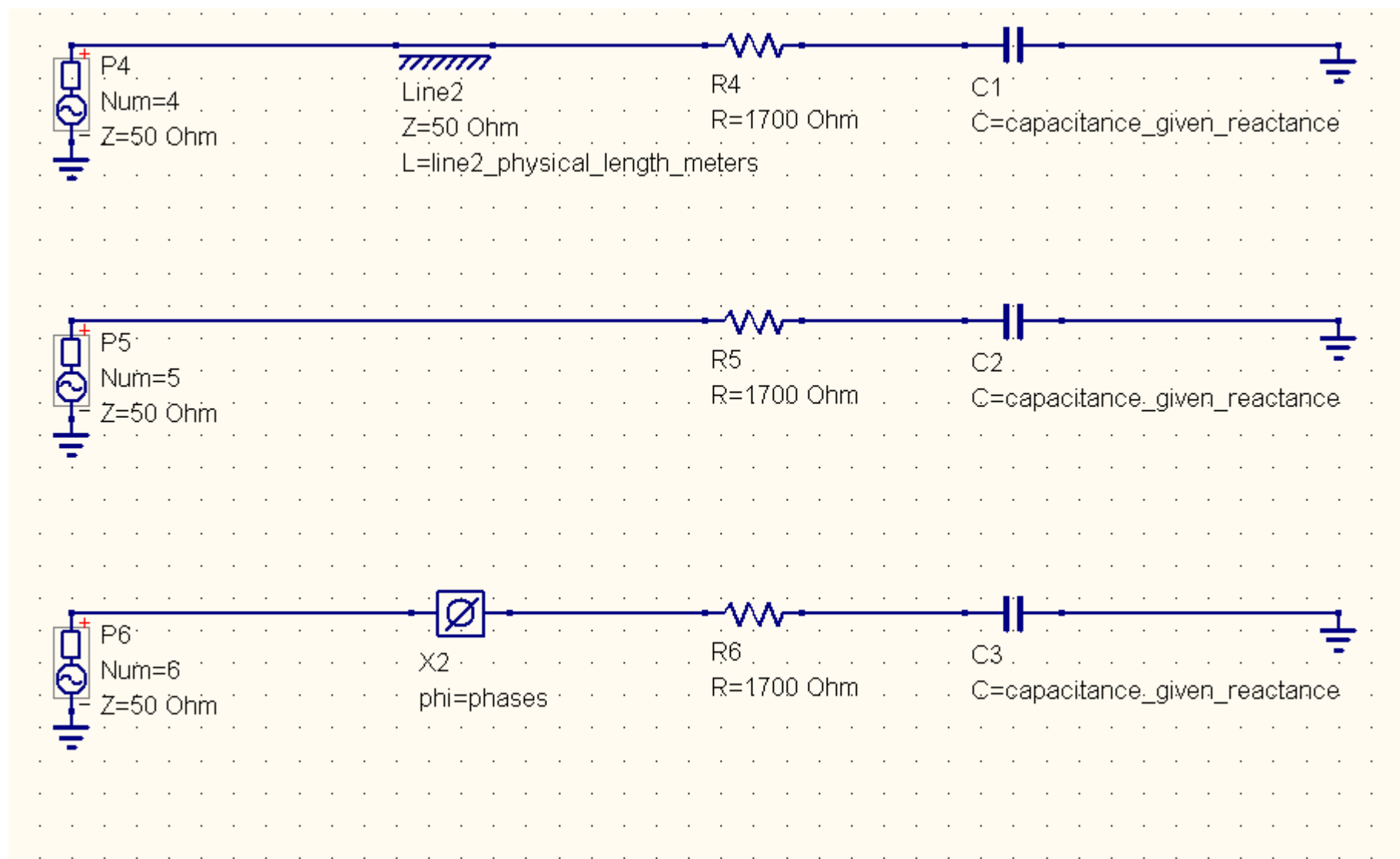PC SIMULATION: SCHEMATIC 14.110 MHz, 1700 - j 1500 Ohm



RESULTS: SMITH CHART PLOT 14.110 MHz

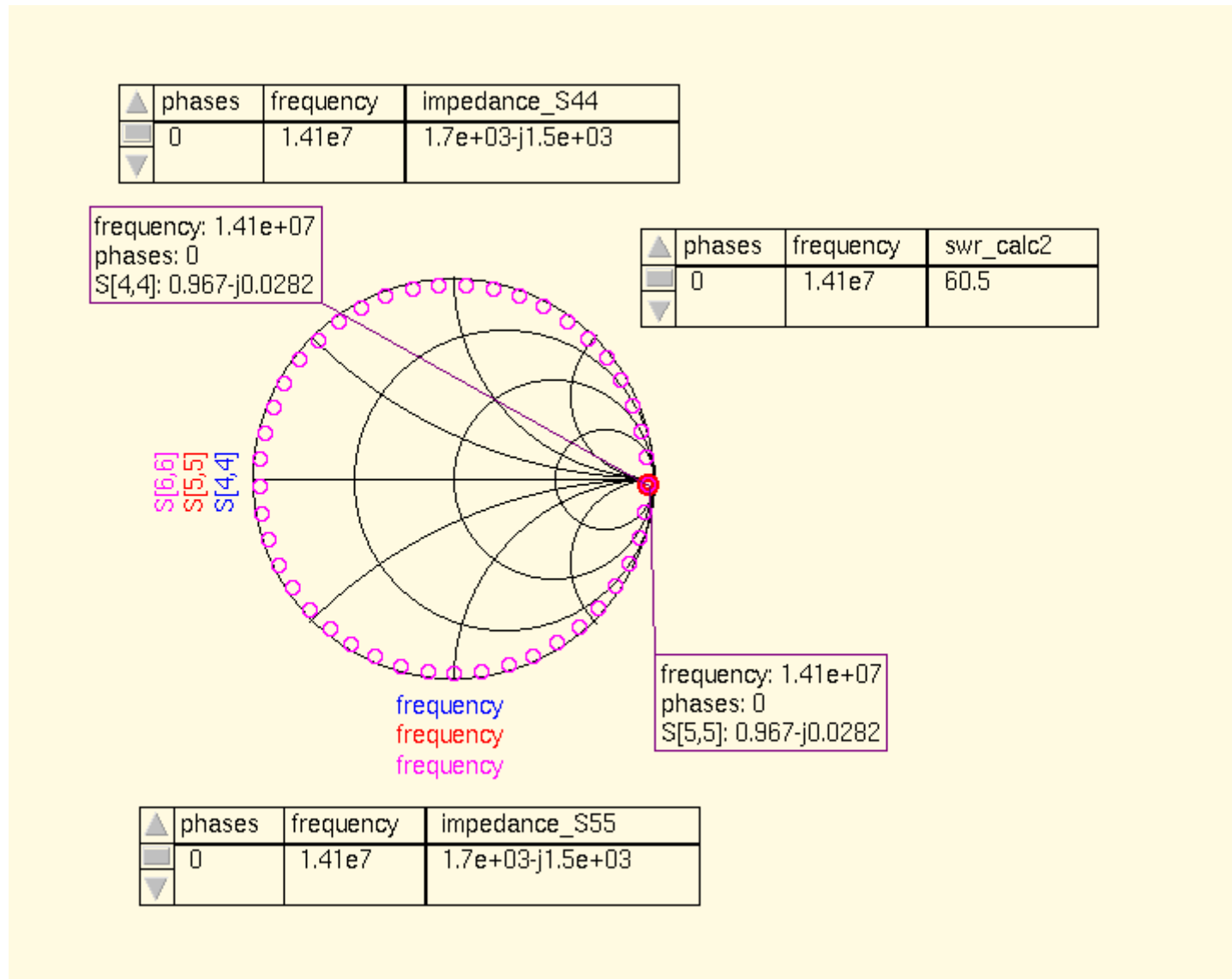

Matching this impedance to 50 ohms would be a challenge.
 SWR 60:1

PC SIMULATION: SCHEMATIC 18.110 MHz, 120 – j 500 Ohms

Equation

Eqn2

capacitance_given_reactance= $1/(2*\pi*carrier2_frequency_MHz*1E6*reactanceC_ohm)$

carrier2_frequency_MHz=18.110

line2_physical_length_meters=0*wavelength_air_meters


reactanceC_ohm=500

swr_calc2=rtoswr(S[6,6])

impedance_S44=rtoz(S[4,4])

impedance_S55=rtoz(S[5,5])

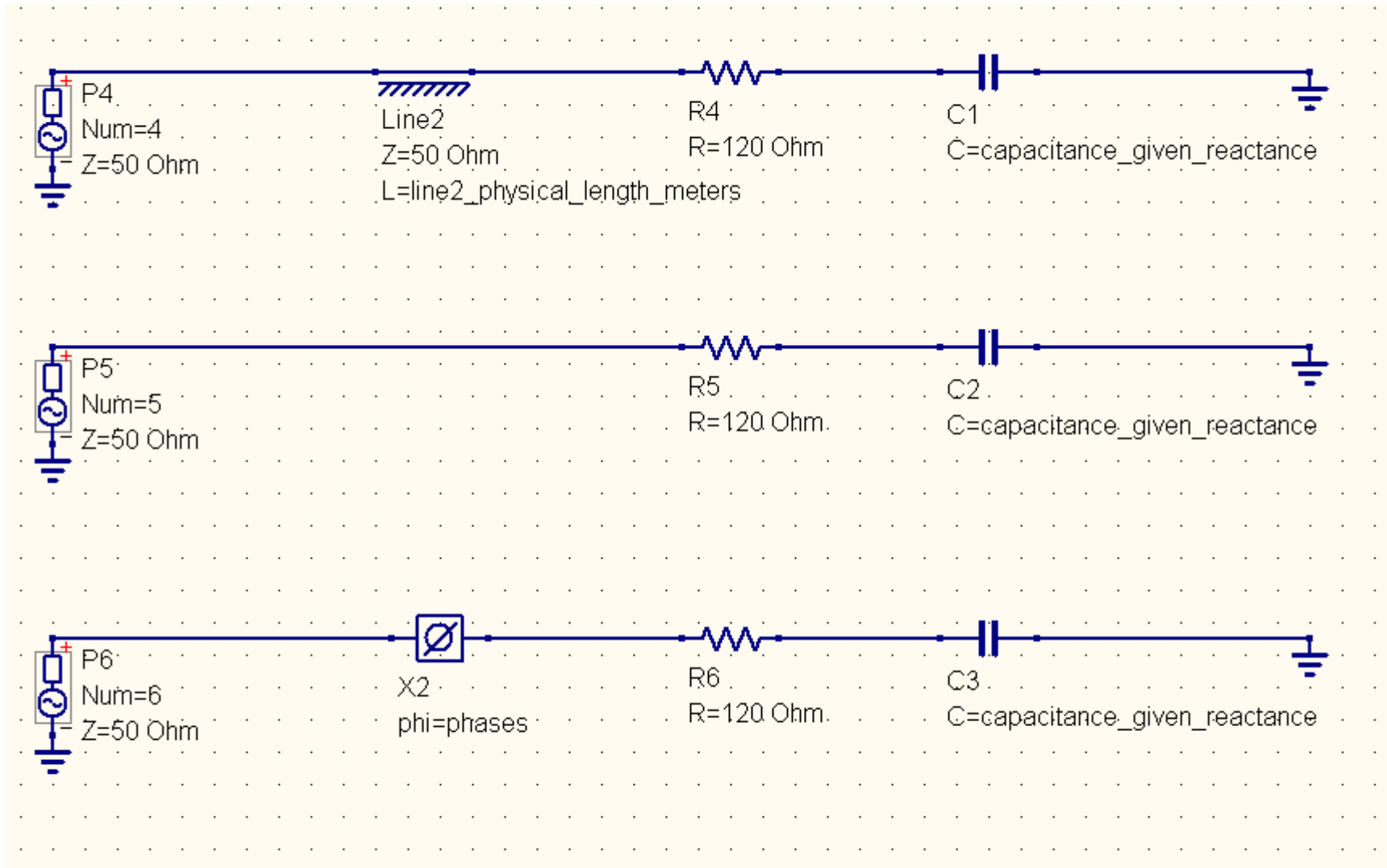PC SIMULATION: SCHEMATIC 18.110 MHz, 120 - j 500 Ohms



RESULTS: SMITH CHART PLOT 18.110 MHz


▲	phases	frequency	impedance_S44
■	0	1.81e7	120-j500
▼			

frequency: 1.81e+07
 phases: 0
 S[4,4]: 0.939-j0.179

▲	phases	frequency	swr_calc2
■	0	1.81e7	44.5
▼			

Need to match to here.

S[6,6]
 S[5,5]
 S[4,4]

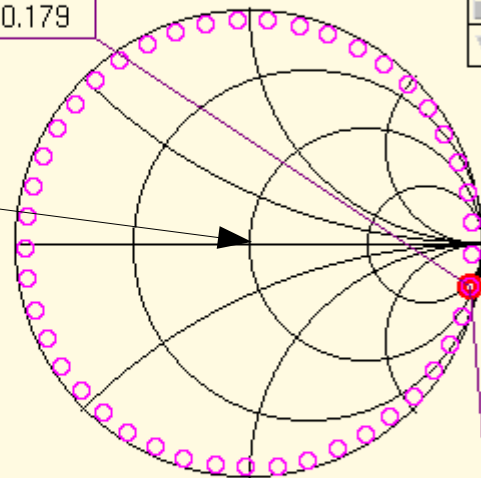

frequency
 frequency
 frequency

frequency: 1.81e+07
 phases: 0
 S[5,5]: 0.939-j0.179

▲	phases	frequency	impedance_S55
■	0	1.81e7	120-j500
▼			

Matching this impedance to 50 ohms is not as severe as 14.11MHz. Here SWR 44:1. Try to design an L-C network.

PC SIMULATION: MATCHING NETWORK 18.110 MHz

S parameter simulation

SP1
Type=const
Values=[18.11 MHz]

Parameter sweep


SW1
Sim=SP1
Type=lin
Param=phases
Start=0
Stop=180
Points=46

Equation

Eqn2
capacitance_given_reactance= $1/(2*\pi*carrier2_frequency_MHz*1E6*reactanceC_ohm)$
carrier2_frequency_MHz=18.110
line2_physical_length_meters=0*wavelength_air_meters
reactanceC_ohm=500
swr_calc2=rtoswr(S[6,6])
impedance_S44=rtoz(S[4,4])
impedance_S55=rtoz(S[5,5])


PC SIMULATION: MATCHING NETWORK 18.110 MHz

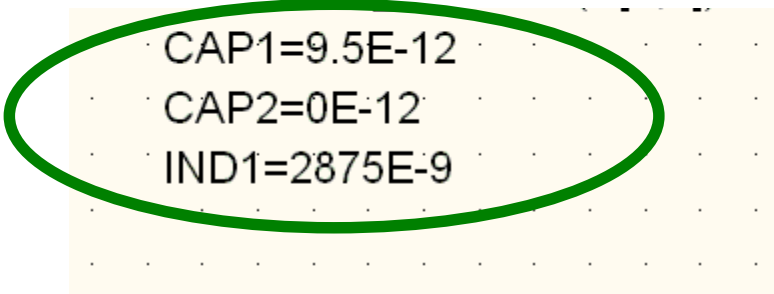Trial and error values of inductance and capacitance that produce a match for 18.110 MHz. Circuit shown on following page.




```
CAP1=9.5E-12  
CAP2=0E-12  
IND1=2875E-9
```

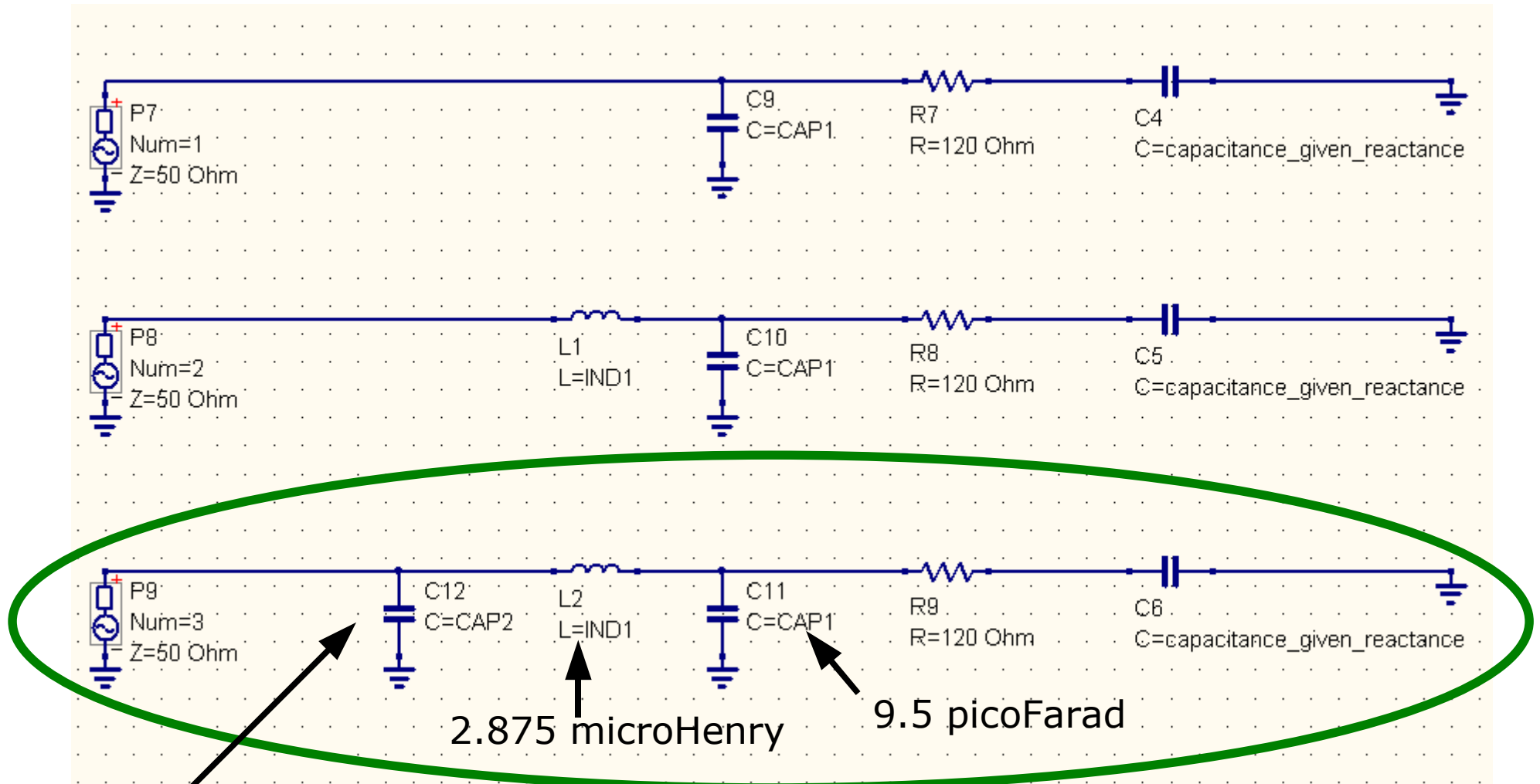
PC SIMULATION: MATCHING NETWORK 18.110 MHz



Zero picoFarad (in a real tuner, the radio-side variable capacitor is set to its minimum value)

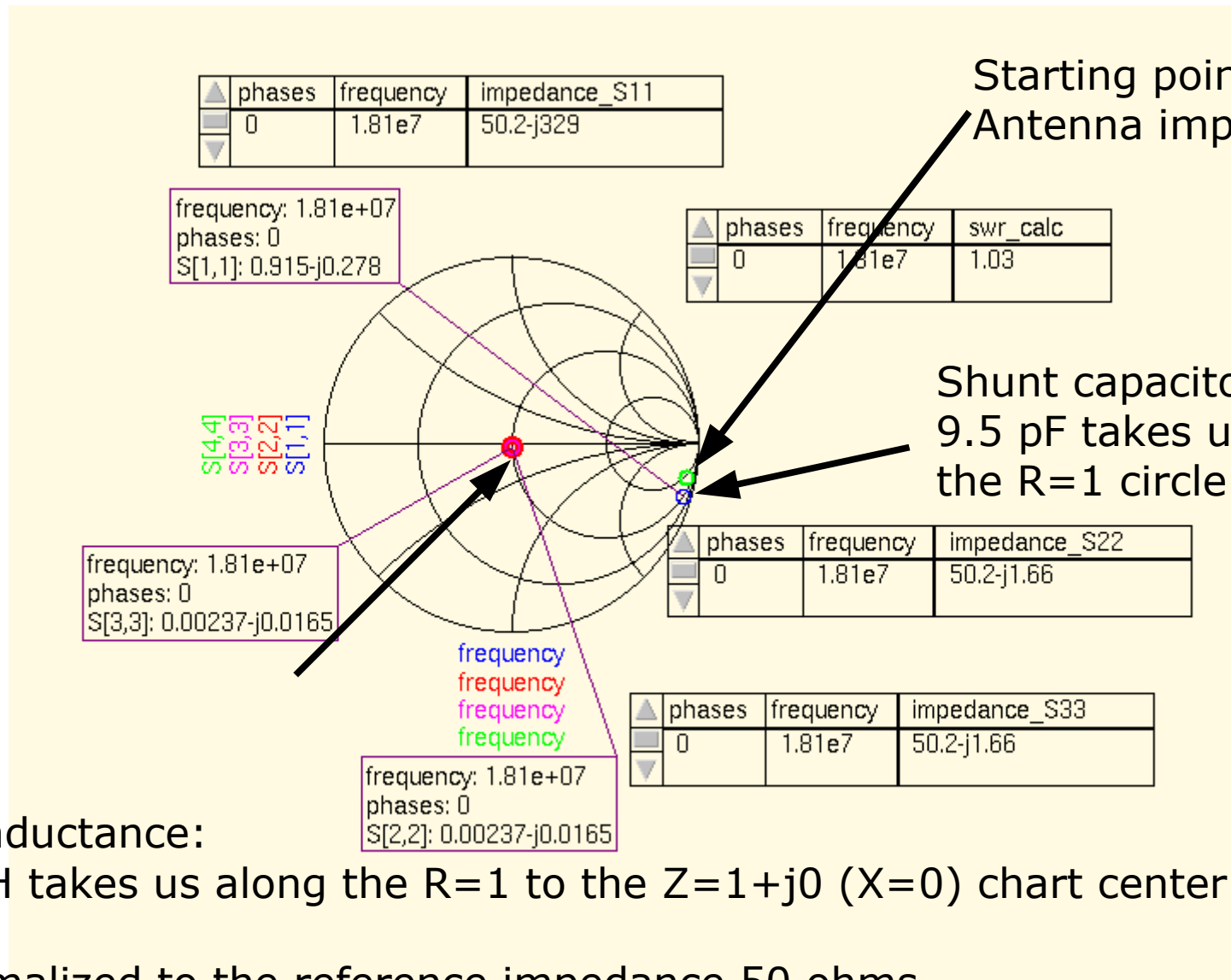RESULTS: SMITH CHART PLOT 18.110 MHz MATCHED



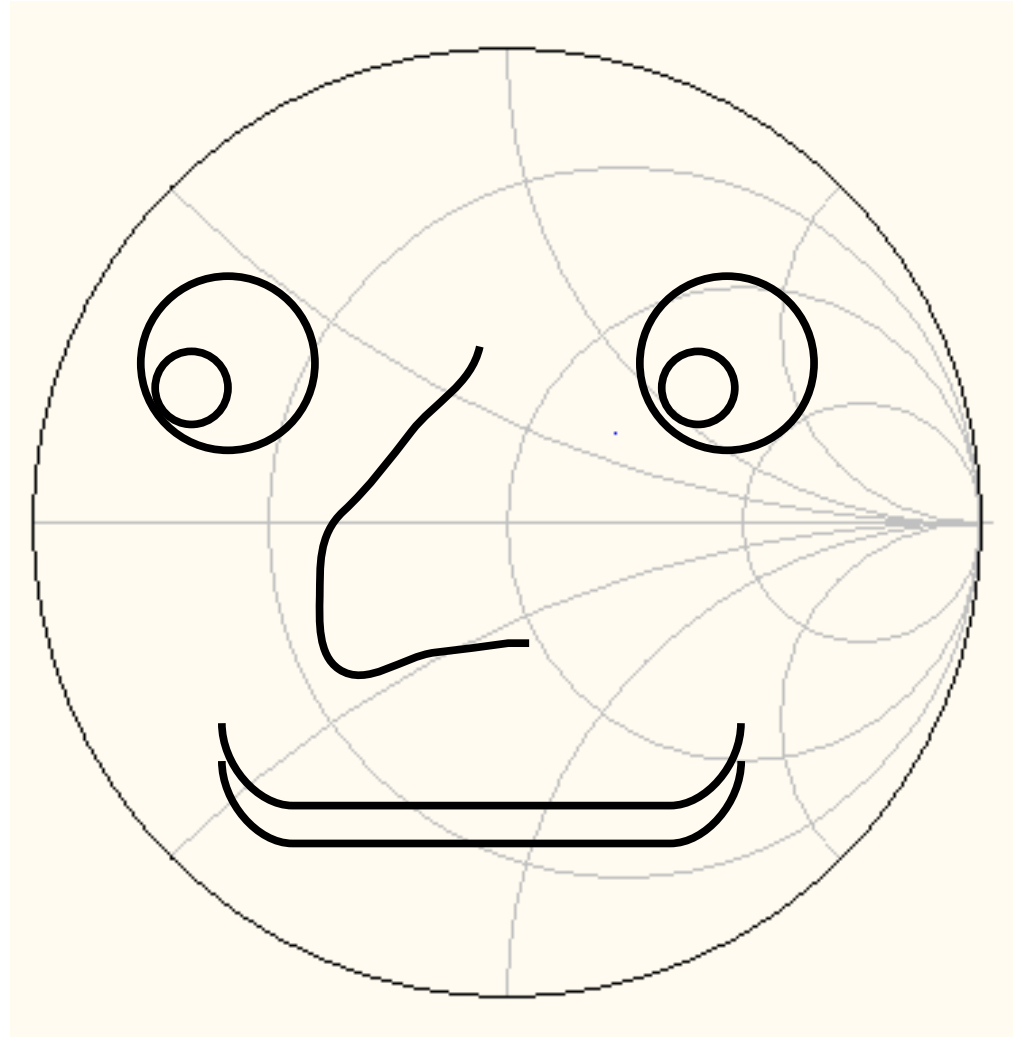

THANKS!